

24	10/29	11/2			Design a circuit for the state diagram handed out in class.
					There is one input, X, and one output, Y. Use D flip-flops.
					Check your circuit to ensure that it is self correcting.

